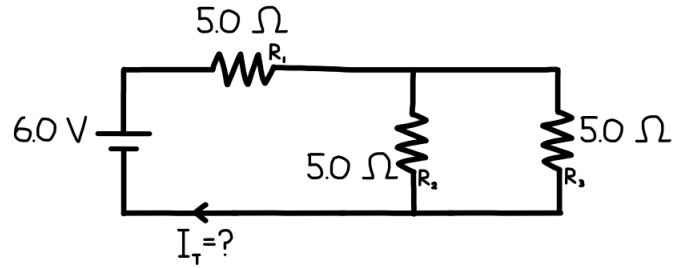


2- Combination Circuits


- 1) A **6.0 V DC battery** is connected to a circuit consisting of **three resistors**, as shown in the diagram.



- $R_1 = 5.0 \Omega$ is connected **in series** with a parallel combination of:
 - $R_2 = 5.0 \Omega$
 - $R_3 = 5.0 \Omega$

- (a) Determine the **equivalent resistance** of the parallel section containing R_2 and R_3 .
- (b) Determine the **total resistance** of the circuit.
- (c) Determine the **total current** supplied by the battery.
- (d) Determine the **current through** R_1 .
- (e) Determine the **current through** R_2 and R_3 .
- (f) Determine the **voltage drop across each resistor**.

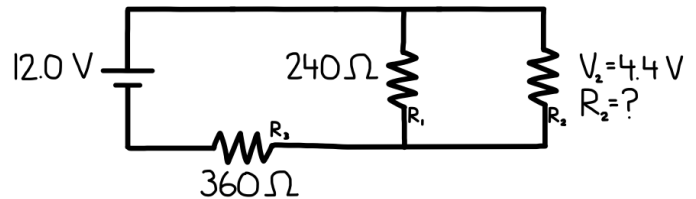- 2) A **12.0 V DC battery** is connected to a circuit consisting of **three resistors**, as shown in the diagram.




- $R_3 = 360 \Omega$ is connected **in series** with a parallel combination of:
 - $R_1 = 240 \Omega$
 - R_2 , whose resistance is **unknown**
 - The **voltage drop across** R_2 is $V_2 = 4.4 \text{ V}$

- (a) Determine the **voltage across the parallel section** of the circuit.
- (b) Determine the **current through** R_1 .
- (c) Determine the **current through** R_2 .
- (d) Determine the **resistance of** R_2 .
- (e) Determine the **equivalent resistance** of the parallel section.
- (f) Determine the **total resistance** of the circuit.
- (g) Determine the **total current** supplied by the battery.

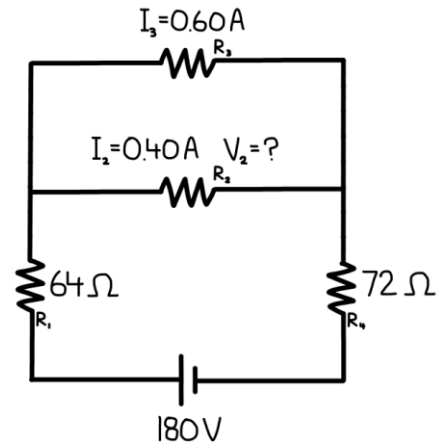3) A **180 V DC power source** is connected to a circuit consisting of **four resistors**, arranged as shown in the diagram.


- $R_1 = 64 \Omega$ and $R_4 = 72 \Omega$ are connected **in series** with the rest of the circuit.
- Between the top and bottom nodes, there are **two resistors in parallel**:
 - R_2 , carrying a current of $I_2 = 0.40 \text{ A}$
 - R_3 , carrying a current of $I_3 = 0.60 \text{ A}$



- Determine the **total current** supplied by the power source.
- Determine the **voltage across the parallel section** of the circuit.
- Determine the **voltage across R_2** .
- Determine the **resistance of R_2** .
- Determine the **resistance of R_3** .
- Verify that your results are consistent with **Ohm's Law** and the rules for **series-parallel circuits**.

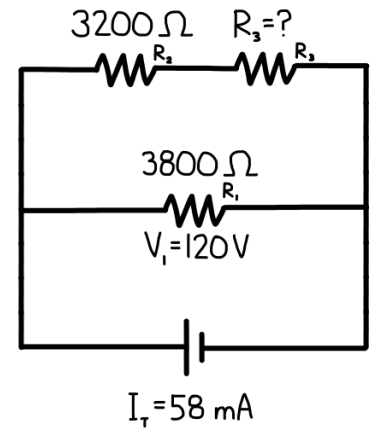
4) A DC power source is connected to a circuit consisting of **three resistors**, arranged as shown in the diagram.

- The **total current** supplied by the source is $I_{\text{total}} = 58 \text{ mA}$
- One branch contains a single resistor:
 - $R_1 = 3800 \Omega$
 - The voltage across this resistor is $V_1 = 120 \text{ V}$
- The other branch contains **two resistors in series**:
 - $R_2 = 3200 \Omega$
 - R_3 , whose resistance is **unknown**



- Determine the **voltage of the power source**.
- Determine the **current through R_1** .
- Determine the **current through the branch containing R_2 and R_3** .
- Determine the **voltage across the series combination of R_2 and R_3** .
- Determine the **resistance of R_3** .

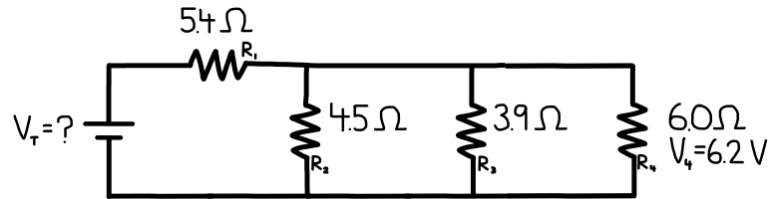5) A circuit consists of a **DC power source** connected to **four resistors**, arranged as shown in the diagram.




- $R_1 = 5.4 \Omega$ is connected **in series** with a parallel network of three resistors:
 - $R_2 = 4.5 \Omega$
 - $R_3 = 3.9 \Omega$
 - $R_4 = 6.0 \Omega$, The **voltage across R_4** is $V_4 = 6.2 \text{ V}$
- The **voltage of the power source**, V_T , is **unknown**.

- (a) Determine the **voltage across the parallel section** of the circuit.
- (b) Determine the **current through R_4** .
- (c) Determine the **current through R_2 and R_3** .
- (d) Determine the **total current entering the parallel section**.
- (e) Determine the **voltage drop across R_1** .
- (f) Determine the **voltage of the power source**, V_T .

Important Instructions


- **Do not substitute numerical values** for R .
- All answers must be expressed **symbolically in terms of R** .
- Final expressions should be **fully simplified**.

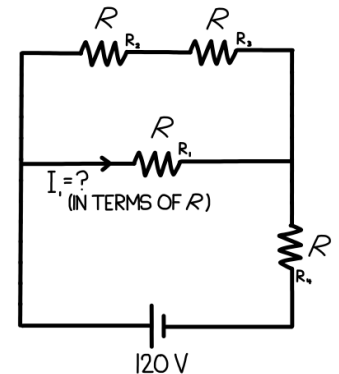6) A **120 V DC power source** is connected to a circuit consisting of **four identical resistors**, each with resistance R , arranged as shown in the diagram.



- (a) Determine the **equivalent resistance** of the top branch in terms of R .
- (b) Determine the **equivalent resistance** of the parallel section in terms of R .
- (c) Determine the **total resistance** of the circuit in terms of R .
- (d) Determine the **total current** supplied by the battery in terms of R .
- (e) Determine the **current through the middle resistor**, I_1 , **in terms of R** .

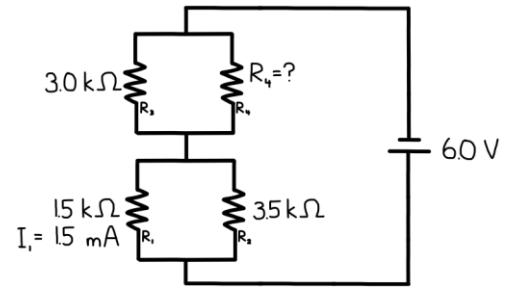- 7) A **6.0 V DC power source** is connected to a circuit consisting of **four resistors**, arranged as shown in the diagram. The circuit is made of **two parallel sections connected in series**:



Lower parallel section

- $R_1 = 15 \text{ k}\Omega$, The current through R_1 is $I_1 = 1.5 \text{ mA}$
- $R_2 = 35 \text{ k}\Omega$

Upper parallel section

- $R_3 = 3.0 \text{ k}\Omega$
- R_4 , whose resistance is **unknown**

- Determine the **voltage across the lower parallel section**.
- Determine the **current through R_2** .
- Determine the **total current** flowing through the circuit.
- Determine the **voltage across the upper parallel section**.
- Determine the **current through R_3** .
- Determine the **resistance of R_4** .

- 8) An **18.0 V DC battery** is connected to a circuit consisting of **four resistors**, arranged as shown in the diagram. The circuit has **two branches in parallel**:


Upper branch

- A resistor $R_2 = 84 \Omega$ is connected **in series** with a parallel combination of:
 - $R_3 = 6.5 \Omega$
 - $R_4 = 4.0 \Omega$

Lower branch

- A single resistor $R_1 = 10.3 \Omega$

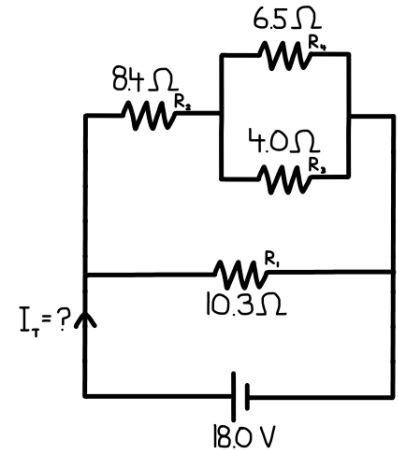The **total current supplied by the battery**, I_T , is unknown.



- Determine the **equivalent resistance of the parallel pair R_3 and R_4** .
- Determine the **total resistance of the upper branch**.
- Determine the **equivalent resistance of the entire circuit**.
- Determine the **total current** supplied by the battery.
- Determine the **current in each branch**.