


More Circuits

1. A DC power source is connected to a circuit consisting of **four resistors**, arranged as shown in the diagram.

- **Resistors R_1 and R_2 are connected in series**, forming one branch of the circuit.
- **Resistors R_3 and R_4 are connected in series**, forming a second branch of the circuit.
- The two series branches are connected **in parallel** with each other.

The following information is known:

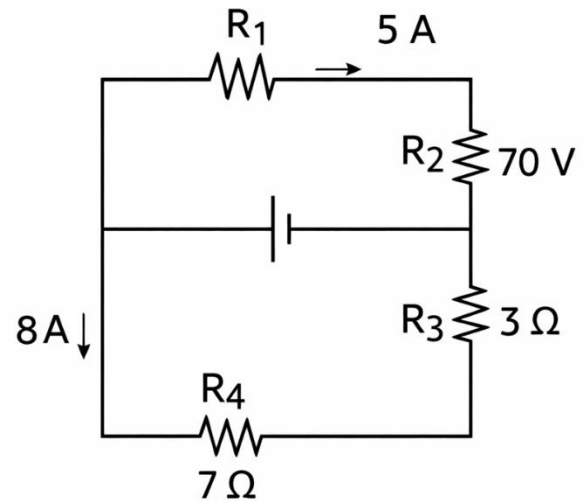- The current through resistor R_1 is $I_{R_1} = 5.0 \text{ A}$
- The current in the left vertical wire below the junction is $I = 8.0 \text{ A}$
- The voltage drop across resistor R_2 is $V_{R_2} = 70 \text{ V}$
- $R_3 = 3.0 \Omega$




- (a) Determine the **current in each branch** of the circuit.
- (b) Determine the **current through R_2** .
- (c) Determine the **resistance of R_2** .
- (d) Determine the **current through R_3 and R_4** .
- (e) Determine the **voltage across each series branch**.
- (f) Determine the **resistance of R_1** .
- (g) Determine the **voltage of the power source**.

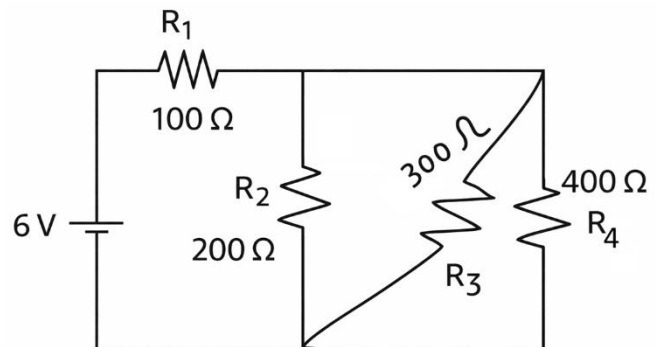2. A **6.0 V DC battery** is connected to a circuit consisting of **four resistors**, arranged as shown in the diagram.

- $R_1 = 100 \Omega$ is connected **in series** with the rest of the circuit.
- After R_1 , the circuit splits into **three parallel branches**:
 - $R_2 = 200 \Omega$
 - $R_3 = 300 \Omega$
 - $R_4 = 400 \Omega$

All three of these resistors are connected between the **same two junctions**, and therefore form a **parallel combination**.



- (a) Determine the **equivalent resistance** of the parallel combination of R_2 , R_3 , and R_4 .
- (b) Determine the **total resistance** of the circuit.
- (c) Determine the **total current** supplied by the battery.
- (d) Determine the **current through each resistor**: R_1 , R_2 , R_3 , and R_4 .
- (e) Determine the **voltage drop across each resistor**.
- (f) Verify that your results are consistent with **Ohm's Law** and the rules for **series and parallel circuits**.

3. An **8.0 V DC battery** is connected to a circuit consisting of **four resistors**, arranged as shown in the diagram.

- $R_1 = 40 \Omega$ is connected **in series** with the rest of the circuit.
- $R_2 = 60 \Omega$ and $R_3 = 120 \Omega$ are connected **in parallel** with each other.
- Resistor $R_4 = 40 \Omega$ is **bypassed by a conducting wire**, creating a short circuit across it.

(a) Explain why R_4 has **no effect** on the behaviour of the circuit.


(b) Determine the **equivalent resistance** of the parallel combination of R_2 and R_3 .

(c) Determine the **total resistance** of the circuit.

(d) Determine the **total current** supplied by the battery.

(e) Determine the **current through** R_2 and R_3 .

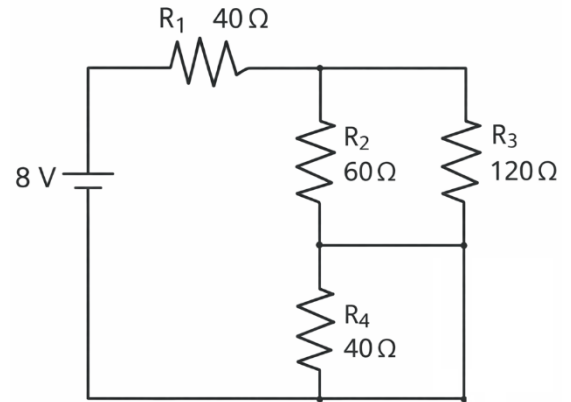(f) Determine the **voltage drop across** R_1 , R_2 , and R_3 .



4. A **12.0 V DC power source** is connected to a circuit consisting of **five resistors**, arranged as shown in the diagram.


• **Lower branch:**

- R_1 is connected in series with R_2 .
- The voltage drop across R_1 is **5.0 V**.
- The current through R_2 is **6.0 A**.

• **Upper branch:**

- A total current of **4.0 A** enters a parallel combination of:
 - R_3 , which carries **3.0 A**
 - R_4 , which has a voltage drop of **8.0 V**
- The parallel combination then reconnects and passes through R_5 in series.

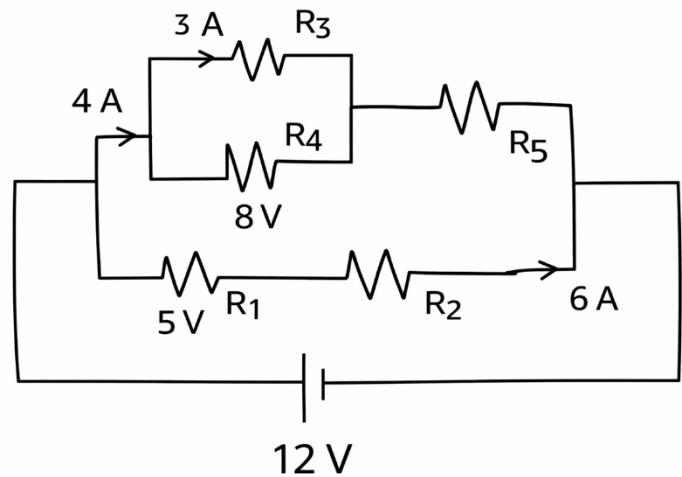• The **upper and lower branches are connected in parallel** between the same two junctions.



(a) Determine the **current through** R_4 .

(b) Determine the **current through** R_5 .

(c) Determine the **resistance of** R_4 .

(d) Determine the **resistance of** R_3 .

(e) Determine the **resistance of** R_1 .


(f) Determine the **resistance of** R_2 .

(g) Determine the **voltage across the upper branch**.

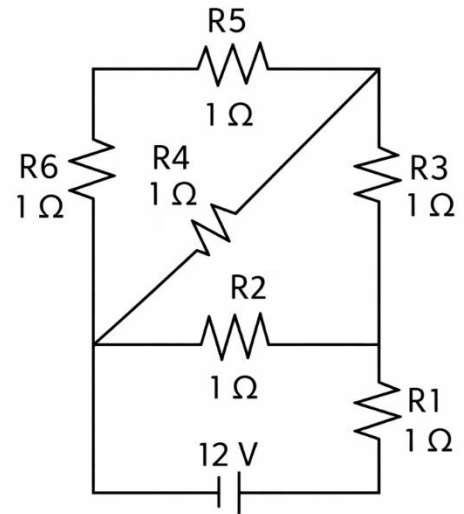5. A **12.0 V DC battery** is connected to a circuit consisting of **six resistors**, arranged as shown in the diagram. All resistors have the **same resistance**:

$$R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 1.0 \Omega$$

- The circuit contains **multiple junctions** and **cannot be reduced** using simple series–parallel rules alone.
- Some resistors connect the **same pairs of nodes**, and symmetry may be used to simplify the analysis.
- Kirchhoff's Laws are required.



- Identify all **unique nodes** in the circuit and label them clearly.
- Determine which resistors (if any) carry **equal currents**, and explain why.
- Determine the **current through each resistor**.
- Determine the **voltage drop across each resistor**.
- Determine the **total current** supplied by the battery.
- Determine the **equivalent resistance** of the circuit.

6. A **100 V DC power source** is connected to a circuit consisting of **nine resistors**, arranged as shown in the diagram. The circuit contains **multiple junctions and loops** and **cannot be simplified** using basic series–parallel reductions alone.


Given information

- $R_1 = 3 \Omega$
- $R_2 = 3 \Omega$
- $R_4 = 2 \Omega$
- $R_5 = 2 \Omega$
- $R_7 = 1 \Omega$
- $R_8 = 1 \Omega$

Additional measurements:

- The **current through R_2** is $I_{R_2} = 6.0 \text{ A}$
- The **voltage drop across R_5** is $V_{R_5} = 6.0 \text{ V}$
- The **current through R_9** is $I_{R_9} = 1.0 \text{ A}$

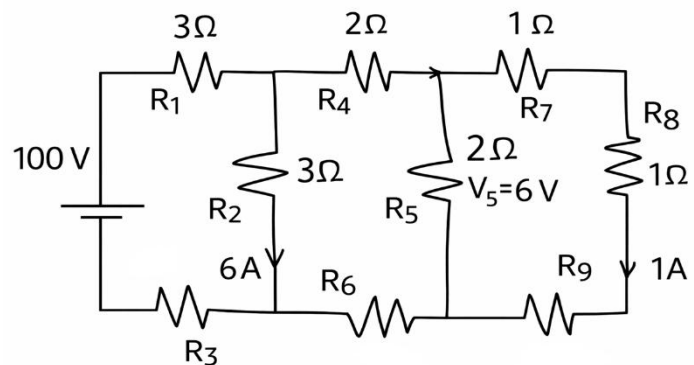The resistances of R_3 , R_6 , and R_9 are **unknown**.



- Identify and clearly label all **junctions (nodes)** in the circuit.
- Determine:
 - the current through R_1
 - the current through R_4
 - the current through R_7
- Determine the **voltage drop across R_2** .
- Determine the **resistance of R_3** .
- Determine the **resistance of R_6** .
- Determine the **resistance of R_9** .
- Determine the **total current supplied by the battery**.

Solutions

1.

$V_T = 80V$	$V_1 = 10V$	$V_2 = 70V$
$I_T = 13A$	$I_1 = 5A$	$I_2 = 5A$
$R_T = 6.15\Omega$	$R_1 = 2\Omega$	$R_2 = 14\Omega$

$V_3 = 24V$	$V_4 = 56V$
$I_3 = 8A$	$I_4 = 8A$
$R_3 = 3\Omega$	$R_4 = 7\Omega$

2.

$V_T = 6V$	$V_1 = 3.12V$	$V_2 = 2.88V$
$I_T = 31.2mA$	$I_1 = 31.2mA$	$I_2 = 14.4mA$
$R_T = 192\Omega$	$R_1 = 100\Omega$	$R_2 = 200\Omega$

$V_3 = 2.88V$	$V_4 = 2.88V$
$I_3 = 9.6mA$	$I_4 = 7.2mA$
$R_3 = 300\Omega$	$R_4 = 400\Omega$

3.

$V_T = 12V$	$V_1 = 5V$	$V_2 = 7V$
$I_T = 10A$	$I_1 = 6A$	$I_2 = 6A$
$R_T = 1.2\Omega$	$R_1 = 0.833\Omega$	$R_2 = 1.167\Omega$

$V_3 = 8V$	$V_4 = 8V$	$V_5 = 4V$
$I_3 = 3A$	$I_4 = 1A$	$I_5 = 4A$
$R_3 = 2.67\Omega$	$R_4 = 8\Omega$	$R_5 = 1\Omega$

4.

$V_T = 8V$	$V_1 = 4V$	$V_2 = 4V$
$I_T = 0.1A$	$I_1 = 0.1A$	$I_2 = 0.067A$
$R_T = 80\Omega$	$R_1 = 40\Omega$	$R_2 = 60\Omega$

$V_3 = 4V$	$V_4 = 0A$
$I_3 = 0.033A$	$I_4 = 0A$
$R_3 = 120\Omega$	$R_4 = 40\Omega$

5.

$V_T = 12V$	$V_1 = 7.38V$	$V_2 = 4.62V$
$I_T = 7.38A$	$I_1 = 7.38A$	$I_2 = 4.62A$
$R_T = 1.625\Omega$	$R_1 = 1\Omega$	$R_2 = 1\Omega$

$V_3 = 2.77V$	$V_4 = 1.85V$
$I_3 = 2.77A$	$I_4 = 1.85A$
$R_3 = 1\Omega$	$R_4 = 1\Omega$

$V_5 = 0.923V$	$V_6 = 0.923V$
$I_5 = 0.923A$	$I_6 = 0.923A$
$R_5 = 1\Omega$	$R_6 = 1\Omega$

6.

$V_T = 100V$	$V_1 = 30V$	$V_2 = 18V$	$V_3 = 52V$	$V_4 = 8V$
$I_T = 10A$	$I_1 = 10A$	$I_2 = 6A$	$I_3 = 10A$	$I_4 = 4A$
$R_T = 10\Omega$	$R_1 = 3\Omega$	$R_2 = 3\Omega$	$R_3 = 5.2\Omega$	$R_4 = 2\Omega$

$V_5 = 6V$	$V_6 = 4V$	$V_7 = 1V$	$V_8 = 1V$	$V_9 = 4V$
$I_5 = 3A$	$I_6 = 4A$	$I_7 = 1A$	$I_8 = 1A$	$I_9 = 1A$
$R_5 = 2\Omega$	$R_6 = 1\Omega$	$R_7 = 1\Omega$	$R_8 = 1\Omega$	$R_9 = 4\Omega$