

Terminal Voltage and Power

Notes for students

- The **terminal voltage** is the voltage across the **external circuit**.
 - The internal resistance of the battery must be included when determining the current.
 - You may use the relationship $V_{\text{terminal}} = \varepsilon - Ir$
-


- 1) A **real battery** with an **emf of 6.0 V** and an **internal resistance of 1.4** is connected to an external circuit, as shown in the diagram.

The external circuit consists of **two resistors connected in series**:

- $R_1 = 8.0$
- $R_2 = 5.0$

Assume all connecting wires have negligible resistance.

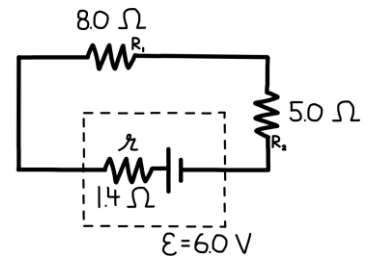Determine the terminal voltage of the battery while the circuit is operating.



Notes for students

- The internal resistance is **in series** with the external resistors.
 - Power dissipated in a resistor can be found using $P = I^2R$
 - The emf of the battery is related to the current and total resistance by $V_{\text{terminal}} = \varepsilon - Ir$
-

- 2) A **real battery** with an **emf of $\varepsilon = 6.04$ V** and an **unknown internal resistance r** is connected to an external circuit, as shown in the diagram.


The external circuit consists of **two resistors connected in series**:

- $R_1 = 1.23 \Omega$
- R_2 , which dissipates power at a rate of $P_2 = 1.337$ W

The **current in the circuit** is measured to be $I = 0.778$ A

Assume all connecting wires have negligible resistance.

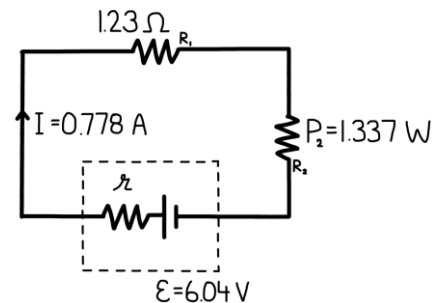Determine the internal resistance r of the battery.



Notes for students

- The internal resistance affects the **current supplied by the cell**, but not the measured voltage across R_1 .
-

3) A real cell with an **internal resistance of $r = 11 \Omega$** is connected to an external circuit, as shown in the diagram. The external circuit consists of **two parallel branches**:


- Upper branch:** two resistors connected in series
 - $R_2 = 66 \Omega$
 - $R_3 = 77 \Omega$

- Middle branch:** a single resistor $R_1 = 88 \Omega$

The **voltage across R_1** is measured to be $V_1 = 150 \text{ V}$

Assume all connecting wires have negligible resistance.

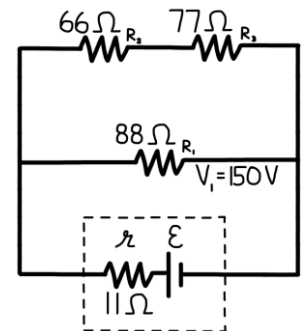Determine the electromotive force (emf), ϵ , of the cell.



Notes for students

- Power dissipated in the internal resistance can be found using $P = I^2 r$
-

4) A real battery with an emf of $\epsilon = 120 \text{ V}$ and an internal resistance r is connected to an external circuit, as shown in the diagram. The external circuit consists of **three resistors connected in parallel**:


- Top resistor: current $I_1 = 0.50 \text{ A}$
- Middle resistor: current $I_2 = 0.30 \text{ A}$
- Bottom resistor: resistance $R_3 = 150 \Omega$

The **terminal voltage of the battery is measured to be 90 V** .

Assume all connecting wires have negligible resistance.

(a) Determine the total current supplied by the battery.

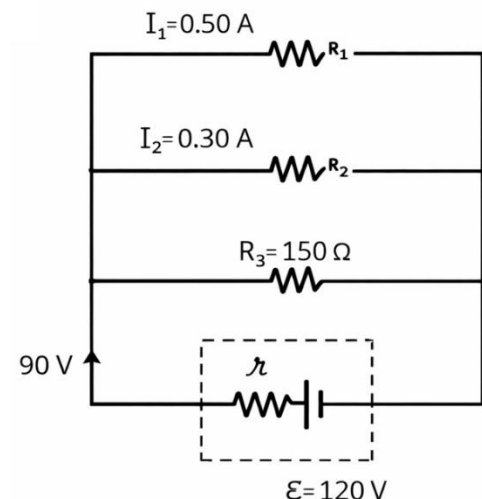(b) Determine the internal resistance r of the battery.



Notes for students

- Power dissipated in the internal resistance can be found using $P = I^2 r$
-


5) A **real battery** with an **emf of $\varepsilon = 110$ V** and an **unknown internal resistance r** is connected to **three external resistors**, arranged as shown in the diagram. The three external resistors are connected **in parallel** and have the following information:

- The current through the **top resistor** is $I_1 = 0.60$ A
- The current through the **middle resistor** is $I_2 = 0.40$ A
- The resistance of the **bottom resistor** is $R_3 = 604$

The **total current supplied by the battery** is: $I_T = 1.15$ A

Assume all connecting wires have negligible resistance.

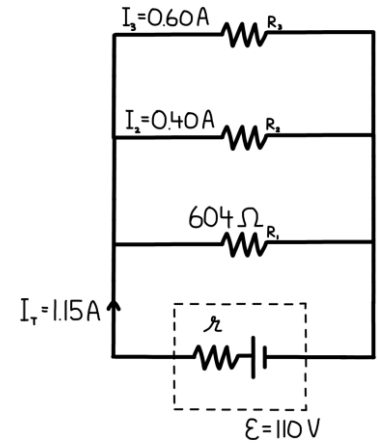- (a) Determine the **internal resistance r** of the battery.
(b) Determine the **power dissipated in the battery's internal resistance**.



Notes for students

- The internal resistance is **in series** with the external circuit.
 - You may use the relationship $V_{\text{terminal}} = \varepsilon - Ir$
-

6) A **power supply** has an **emf of $\varepsilon = 12.0$ V** and an **internal resistance r** . Two experiments are performed using the **same power supply**, as shown in the diagrams.

Experiment 1

The power supply is connected to **one resistor of resistance R** .

- The current delivered by the supply is $I_1 = 9.0$ A



Experiment 2

The same power supply is connected to **two identical resistors**, each of resistance R , **connected in series**.

- The current delivered by the supply is $I_2 = 5.0$ A

Assume all connecting wires have negligible resistance.

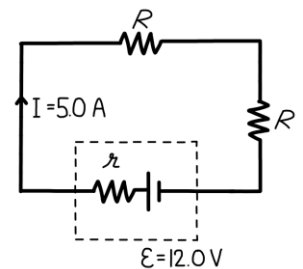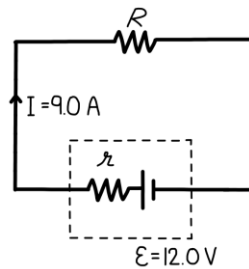Determine the internal resistance r of the power supply.



Notes for students

- Useful relationships: $Q = It$, $P = IV$, $P = I^2R$, $E = Pt$
-

7) A resistor of resistance $R = 40 \Omega$ is connected to a power supply. The current through the resistor is measured to be $I = 0.50 \text{ A}$. Assume the circuit operates continuously for **30 minutes**.

- (a) Determine the power dissipated by the resistor.
(b) Determine the total energy dissipated by the resistor during this time.

8) The circuit consists of **two parallel sections connected in series**:

Upper parallel section

- $R_1 = 6.0 \Omega$
- $R_2 = 45 \Omega$

Lower parallel section

- $R_3 = 20 \Omega$
- R_4 (resistance not specified)

The **current through resistor R_3** is measured to be: $I_1 = 150 \text{ mA}$

Assume all connecting wires have negligible resistance.

- (a) Determine the **amount of electric charge** that flows through resistor R_4 in **1.0 hour**.
(b) Determine the **power dissipated** by resistor R_4 .
(c) Determine the **total energy dissipated** by resistor R_4 during **1.0 hour** of operation.

