

# More Terminal Voltage & Power

## Notes for Students

- The **power dissipated** by a resistor can be calculated using:


$$P = IV \quad \text{or} \quad P = I^2R \quad \text{or} \quad P = \frac{V^2}{R}$$

- In **series circuits**, the current is the same through each component.
- In **parallel circuits**, the voltage across each branch is the same.
- The **brightness of a bulb** depends on the **power** it dissipates.

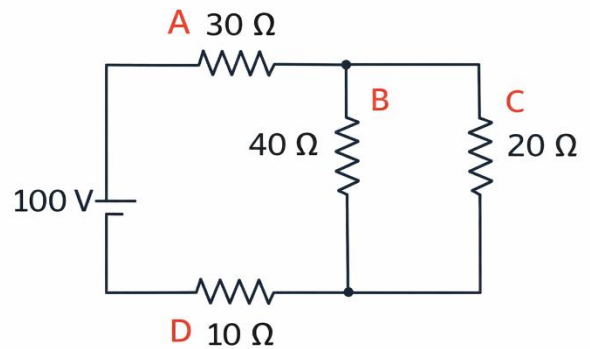- 1) Four **identical light bulbs** are connected to a **100 V power source**, as shown in the diagram. The bulbs have the following resistances: **Bulb A: 30 Ω**, **Bulb B: 40 Ω**, **Bulb C: 20 Ω**, **Bulb D: 10 Ω**

The circuit has the following structure:

- Bulbs **B** and **C** are connected **in parallel** with each other.
- This parallel combination is connected **in series** with bulbs **A** and **D**.



- (a) Determine the **current through each bulb**.
- (b) Determine the **power dissipated by each bulb** (A, B, C, and D).
- 2) The circuit from **Question 1** is modified by adding a **fifth bulb** that is **identical to bulb B**.
- The new bulb is connected **in parallel** with bulbs B and C.
  - All other aspects of the circuit remain unchanged.
- (a) Determine the **new equivalent resistance** of the parallel section.
- (b) Determine the **total current supplied by the power source** in the modified circuit.

- 3) Using the **modified circuit** from Question 2:

For **each bulb**, indicate how its brightness changes compared to the original circuit in Question 1.

brighter     dimmer     the same

- Bulb A:  brighter  dimmer  the same
- Bulb D:  brighter  dimmer  the same
- Bulb B:  brighter  dimmer  the same
- Bulb C:  brighter  dimmer  the same

(Explain your reasoning clearly, referring to:)


- how the **total resistance** of the circuit changes
- how **current and voltage** behave in series and parallel sections
- the relationship between **power and brightness**

- 4) A real battery with an emf of  $\varepsilon = 9.0$  V and an internal resistance of  $r = 1.0$  is connected to an external circuit, as shown in the diagram.

The external circuit consists of **two branches connected in parallel**:

- **Upper branch:** two resistors in series,  $40\ \Omega$  and  $50\ \Omega$
- **Lower branch:** a single resistor  $60\ \Omega$

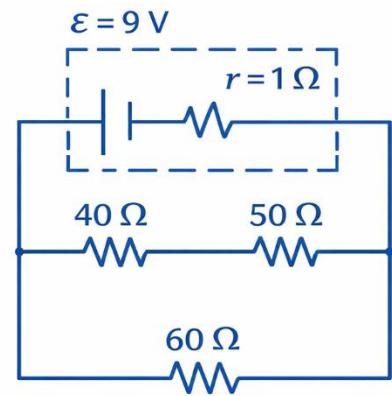Determine the terminal voltage of the battery.




- 5) A real battery with an emf of  $\varepsilon = 6.0$  V and an internal resistance of  $r = 20\ \Omega$  is connected to an external circuit, as shown in the diagram.

The external circuit consists of **two parallel sections connected in series**:

- **Upper parallel section,**  $50\ \Omega$  and  $100\ \Omega$
- **Lower parallel section**  $150\ \Omega$  and  $200\ \Omega$

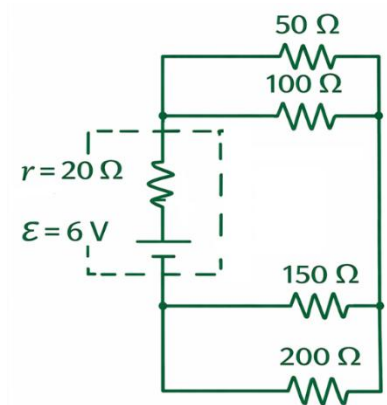Determine the terminal voltage of the battery.



- 6) A real battery with an emf of  $\varepsilon = 18.0$  V is connected to an external circuit, as shown in the diagram. The external circuit consists of **two resistors connected in parallel**:

- Upper branch resistor:  $R_1 = 12\ \Omega$
- Lower branch resistor:  $R_2 = 6.0\ \Omega$

The **terminal voltage of the battery is measured to be 12.0 V** while the circuit is operating.

Assume:

- All connecting wires have negligible resistance
- The battery's internal resistance  $r$  is in series with the external circuit

- Determine the **equivalent resistance** of the external circuit.
- Determine the **total current supplied by the battery**.
- Determine the **internal resistance  $r$**  of the battery.

- 7) A **heating coil** with a resistance of  $10\ \Omega$  is connected to a **120 V power supply**. The coil is immersed in a container holding **2.0 L of water**. The water initially has a temperature of **20 °C**.


Additional information:

- The **specific heat capacity of water** is  $c = 4.18\ \text{J}/(\text{g}^\circ\text{C})$
- Assume:
  - All electrical energy from the coil goes into heating the water
  - No heat is lost to the surroundings
  - The density of water is  $1.0\ \text{g}/\text{mL}$

- Determine the **time required** for the heating coil to raise the temperature of the water to **100 °C**.
- Electricity costs **\$0.11 per kWh**. Determine the **cost** to heat the water from **20 °C to 100 °C**.

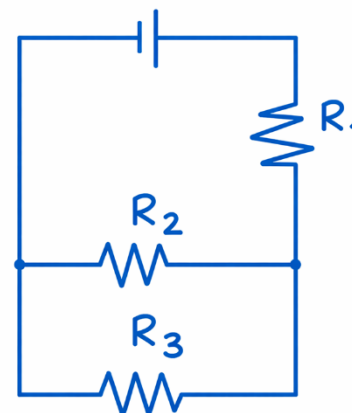8) The circuit shown consists of **three identical resistors**, labeled  $R_1$ ,  $R_2$ , and  $R_3$ , connected to an **ideal battery**, as shown in the diagram.

- Resistor  $R_1$  is connected on the **right-hand vertical branch**.
- Resistors  $R_2$  and  $R_3$  are connected next in parallel on **separate horizontal branches**.
- The battery is connected across the **top of the circuit**.



Assume:

- All resistors have the **same resistance  $R$**
- The battery and connecting wires are **ideal**
- No energy is lost outside the resistors

(a) Determine the **power dissipated** by each resistor:  $P_1$ ,  $P_2$ , and  $P_3$ .


(b) **Compare the power outputs** of the three resistors by writing your answer as ratios (for example,  $P_1 = 2P_2$  or  $P_1 = P_2 = P_3$ ).

(c) Briefly **explain your reasoning**, referring to:

- which resistors share the **same current**
- which resistors share the **same voltage**
- the relationship between **power, current, and voltage**

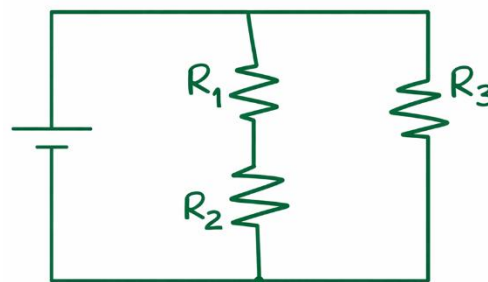9) The circuit shown consists of **three identical resistors**, labeled  $R_1$ ,  $R_2$ , and  $R_3$ , connected to an **ideal battery**, as shown in the diagram.

- Resistors  $R_1$  and  $R_2$  are connected **in series** on the **middle vertical branch** of the circuit.
- Resistor  $R_3$  is connected on the **right-hand vertical branch**.
- The **series combination  $R_1 + R_2$**  is connected **in parallel** with resistor  $R_3$ .
- The battery is connected across the **top and bottom nodes** of the circuit.



Assume:

- All resistors have the **same resistance  $R$**
- The battery and connecting wires are **ideal**
- No energy is lost outside the resistors

(a) Determine the **power dissipated** by each resistor:  $P_1$ ,  $P_2$ , and  $P_3$ .


(b) **Compare the power outputs** of the three resistors by writing your answer as ratios (for example,  $P_1 = 2P_2$  or  $P_1 = P_2 = P_3$ ).

(c) Briefly **explain your reasoning**, referring to:

- which resistors share the **same current**
- which resistors share the **same voltage**
- the relationship between **power, current, and voltage**

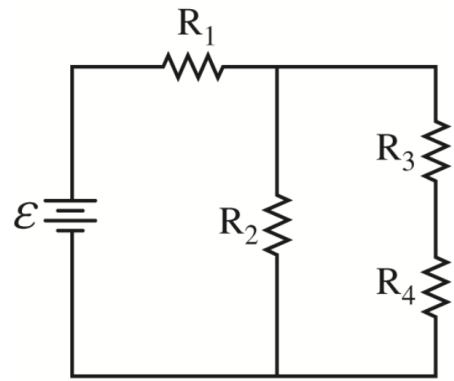10) A circuit consists of an **ideal battery** with emf  $\mathcal{E}$  connected to **four identical resistors**, each with resistance  $R$ , arranged as shown in the diagram.

- $R_1$  is connected **in series** with the rest of the circuit.
- After  $R_1$ , the circuit splits into **two parallel branches**:
  - One branch contains a **single resistor**  $R_2$ .
  - The other branch contains **two resistors**  $R_3$  and  $R_4$  **connected in series**.
- The two branches then rejoin and return to the battery.




Assume:

- All resistors have resistance  $R$
- The battery and connecting wires are ideal
- All results should be expressed **symbolically** in terms of  $\mathcal{E}$  and  $R$

- Derive an expression for the **current**  $I_1$  through resistor  $R_1$ .
- Derive an expression for the **current**  $I_3$  through resistor  $R_3$ .
- Derive an expression for the **total power dissipated** in the circuit.

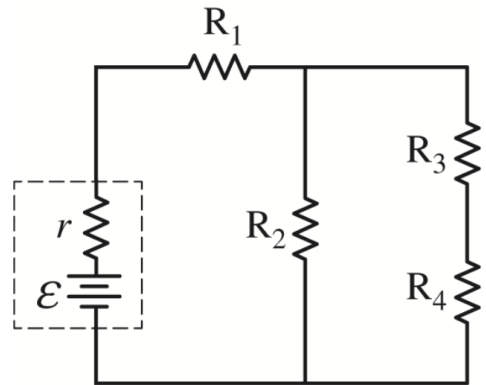11) A circuit consists of **four identical resistors**, labeled  $R_1, R_2, R_3,$  and  $R_4$ , arranged as shown in the diagram.

- $R_1$  is connected **in series** with the rest of the circuit.
- After  $R_1$ , the circuit splits into **two parallel branches**:
  - One branch contains a **single resistor**  $R_2$ .
  - The other branch contains **two resistors**,  $R_3$  and  $R_4$ , **connected in series**.
- The branches rejoin and return to the battery.



#### Original Circuit

- The circuit is first connected to an **ideal battery** (no internal resistance).
- The **total power dissipated** in the resistors is  $P_{\text{original}}$

#### Modified Circuit

- The ideal battery is then replaced with a **non-ideal battery** having:
  - an emf  $\mathcal{E}$
  - an **internal resistance**  $r$ , as shown in the dashed box in the diagram
  - The **total power dissipated in the circuit** is now  $P_{\text{new}}$

Is  $P_{\text{new}}$  **greater than, less than, or equal to**  $P_{\text{original}}$ ?

greater than     less than     equal to

**Explain your reasoning clearly**, referring to:

- how the internal resistance affects the **total current**
- how power depends on current and resistance
- where energy is dissipated in each case